



Instituto Politécnico Nacional

Escuela Superior de Cómputo

Práctica 6 - Archivo de Registros

Unidad de aprendizaje: Arquitectura de Computadoras

Grupo: 3CV1

Alumno(a):

Ramos Diaz Enrique

Profesor(a):

Vega García Nayeli

1 de abril 2020

Índice

1	Código de implementación	2
1.1	Registro	2
1.2	Multiplexor de 16 canales	2
1.3	Demultiplexor de 16 canales de salida	3
1.4	Barrel-Shifter	5
1.5	Multiplexor de 2 canales	6
1.6	Archivo de Registros	7
2	Código de simulación	10
2.1	Registro	10
2.2	Demultiplexor de 16 canales de salida	11
2.3	Barrel-Shifter	13
2.4	Archivo de Registros	14
3	Simulación	18
3.1	Registro	18
3.2	Demultiplexor de 16 canales de salida	18
3.3	Barrel-Shifter	18
3.3.1	Corrimiento a la izquierda	18
3.3.2	Corrimiento a la derecha	19
3.4	Archivo de Registros	19
3.4.1	Archivo entrada: Estimulos.txt	20
3.4.2	Archivo salida: Resultados.txt	20
4	Diagramas RTL	21
4.1	Análisis RTL	21
4.1.1	Registro	21
4.1.2	Multiplexor de 16 canales	21
4.1.3	Demultiplexor de 16 canales de salida	22
4.1.4	Barrel-Shifter	22
4.1.5	Multiplexor de 2 canales	22
4.1.6	Archivo de Registros	23
4.2	Synthesis	25
4.2.1	Registro	25
4.2.2	Multiplexor de 16 canales	26
4.2.3	Demultiplexor de 16 canales de salida	27
4.2.4	Barrel-Shifter	28
4.2.5	Multiplexor de 2 canales	29
4.2.6	Archivo de Registros	30

1. Código de implementación

1.1. Registro

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Registro is
5     generic ( n : integer := 16 );
6     Port ( d : in STD_LOGIC_VECTOR (n-1 downto 0);
7           q : out STD_LOGIC_VECTOR (n-1 downto 0);
8           clr, clk, l : in STD_LOGIC);
9 end Registro;
10
11 architecture Behavioral of Registro is
12 begin
13     process(clk, clr)
14     begin
15         if (clr = '1') then
16             q <= (others => '0');
17         elsif (rising_edge(clk)) then
18             if (l = '1') then
19                 q <= d;
20             end if;
21         end if;
22     end process;
23 end Behavioral;
```

1.2. Multiplexor de 16 canales

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Multiplexor is
5     Port ( c10, c11, c12, c13, c14, c15, c16, c17, c18, c19, c110, c111,
6           ↪ c112, c113, c114, c115 : in STD_LOGIC_VECTOR (15 downto 0);
7           sel : in STD_LOGIC_VECTOR (3 downto 0);
8           salida : out STD_LOGIC_VECTOR (15 downto 0));
9 end Multiplexor;
10
11 architecture Behavioral of Multiplexor is
12 begin
13     with sel select salida <=
```

```
13         cl0 when "0000",
14         cl1 when "0001",
15         cl2 when "0010",
16         cl3 when "0011",
17         cl4 when "0100",
18         cl5 when "0101",
19         cl6 when "0110",
20         cl7 when "0111",
21         cl8 when "1000",
22         cl9 when "1001",
23         cl10 when "1010",
24         cl11 when "1011",
25         cl12 when "1100",
26         cl13 when "1101",
27         cl14 when "1110",
28         cl15 when others;
29 end Behavioral;
```

1.3. Demultiplexor de 16 canales de salida

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Demultiplexor is
5      Port ( d : in STD_LOGIC;
6            l : out std_logic_vector(15 downto 0);
7            sel : in STD_LOGIC_VECTOR (3 downto 0));
8  end Demultiplexor;
9
10 architecture Behavioral of Demultiplexor is
11 begin
12     process(d, sel)
13     begin
14         case sel is
15             when "0000" =>
16                 l <= (others => '0');
17                 l(0) <= d;
18             when "0001" =>
19                 l <= (others => '0');
20                 l(1) <= d;
21             when "0010" =>
22                 l <= (others => '0');
23                 l(2) <= d;
```

```
24     when "0011" =>
25         l <= (others => '0');
26         l(3) <= d;
27     when "0100" =>
28         l <= (others => '0');
29         l(4) <= d;
30     when "0101" =>
31         l <= (others => '0');
32         l(5) <= d;
33     when "0110" =>
34         l <= (others => '0');
35         l(6) <= d;
36     when "0111" =>
37         l <= (others => '0');
38         l(7) <= d;
39     when "1000" =>
40         l <= (others => '0');
41         l(8) <= d;
42     when "1001" =>
43         l <= (others => '0');
44         l(9) <= d;
45     when "1010" =>
46         l <= (others => '0');
47         l(10) <= d;
48     when "1011" =>
49         l <= (others => '0');
50         l(11) <= d;
51     when "1100" =>
52         l <= (others => '0');
53         l(12) <= d;
54     when "1101" =>
55         l <= (others => '0');
56         l(13) <= d;
57     when "1110" =>
58         l <= (others => '0');
59         l(14) <= d;
60     when others =>
61         l <= (others => '0');
62         l(15) <= d;
63     end case;
64 end process;
65 end Behavioral;
```

1.4. Barrel-Shifter

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity BarrelShifter is
5      generic ( n : integer := 16;
6                corr : integer := 4);
7      Port ( dato : in STD_LOGIC_VECTOR (n-1 downto 0);
8            res : out STD_LOGIC_VECTOR (n-1 downto 0);
9            shamt : in STD_LOGIC_VECTOR (corr-1 downto 0);
10           direccion : in STD_LOGIC);
11 end BarrelShifter;
12
13 architecture Behavioral of BarrelShifter is
14 begin
15     process(dato, shamt, direccion)
16         variable aux : std_logic_vector(n-1 downto 0);
17     begin
18         aux := dato;
19         for i in 0 to corr-1 loop
20             if (shamt(i) = '0') then
21                 aux := aux;
22             else
23                 case direccion is
24                     when '1' => --- izquierda
25                         for j in n-1 downto 0 loop          --el ciclo for
26                             -- para el corrimiento a la izquierda
27                             if (j < 2**i) then                --va del mas
28                                 -- significativo al menos significativo
29                                 aux(j) := '0';                --para que los
30                                 -- bits se vayan arrastrando y que los
31                                 -- ultimos
32                             else                                --en
33                                 -- actualizarse sean los de la derecha que es
34                                 -- en donde se ingrean
35                                 aux(j) := aux(j-2**i);        --los 0s por el
36                                 -- corrimiento, si lo recorremos a la
37                                 -- inversa, se actualizaria
38                             end if;                            --primero el bit
39                                 -- menos significativo y ese valor se
40                                 -- replicaria en todo el vector
41                             end loop;                          --teniendo como
42                                 -- resultado un vector lleno de 0s

```

```

32         when others => --- derecha
33             for j in 0 to n-1 loop                -- invirtiendo
34                 → el for
35                 if (j <= (n-1) - 2**i) then
36                     aux(j) := aux(j+2**i);
37                 else
38                     aux(j) := '0';
39                 end if;
40             end loop;
41         end case;
42     end if;
43 end loop;
44 res <= aux;
45 end process;
46 end Behavioral;

```

1.5. Multiplexor de 2 canales

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Mux2C is
5      generic ( n : integer := 16 );
6      Port ( barrelShifter, write_data : in STD_LOGIC_VECTOR (n-1 downto 0);
7            she : in STD_LOGIC;
8            sal : out STD_LOGIC_VECTOR (n-1 downto 0));
9  end Mux2C;
10
11  architecture Behavioral of Mux2C is
12  begin
13      with she select sal <=
14          barrelShifter when '1',
15          write_data when others;
16  end Behavioral;

```

1.6. Archivo de Registros

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ArchivoRegistros is
5      generic ( i : integer := 4;
6                n : integer := 16);
7      Port ( wr, dir, she, clk, clr : in STD_LOGIC;
8            writeReg, readReg1, readReg2, shamt : in STD_LOGIC_VECTOR (i-1
9              ↪ downto 0);
10           writeData : in STD_LOGIC_VECTOR (n-1 downto 0);
11           readData1, readData2 : out STD_LOGIC_VECTOR (n-1 downto 0));
12 end ArchivoRegistros;
13
14 architecture Behavioral of ArchivoRegistros is
15     component Registro is
16         Port ( d : in STD_LOGIC_VECTOR (n-1 downto 0);
17               q : out STD_LOGIC_VECTOR (n-1 downto 0);
18               clr, clk, l : in STD_LOGIC);
19     end component;
20
21     component Demultiplexor is
22         Port ( d : in STD_LOGIC;
23               l : out std_logic_vector(15 downto 0);
24               sel : in STD_LOGIC_VECTOR (3 downto 0));
25     end component;
26
27     component BarrelShifter is
28         Port ( dato : in STD_LOGIC_VECTOR (n-1 downto 0);
29               res : out STD_LOGIC_VECTOR (n-1 downto 0);
30               shamt : in STD_LOGIC_VECTOR (i-1 downto 0);
31               direccion : in STD_LOGIC);
32     end component;
33
34     component Multiplexor is
35         Port ( c10, c11, c12, c13, c14, c15, c16, c17, c18, c19, c110, c111,
36               ↪ c112, c113, c114, c115 : in STD_LOGIC_VECTOR (15 downto 0);
37               sel : in STD_LOGIC_VECTOR (3 downto 0);
38               salida : out STD_LOGIC_VECTOR (15 downto 0));
39     end component;
40
41     component Mux2C is
```



```
40     Port ( barrelShifter, write_data : in STD_LOGIC_VECTOR (n-1 downto
      ↪ 0);
41         she : in STD_LOGIC;
42         sal : out STD_LOGIC_VECTOR (n-1 downto 0));
43 end component;
44
45 signal auxReadData1, auxL, auxD, auxBS: STD_LOGIC_VECTOR (n-1 downto 0);
46 type matrizQ is array (0 to n-1) of STD_LOGIC_VECTOR (n-1 downto 0);
47 signal auxQ : matrizQ;
48 begin
49     demux : Demultiplexor Port map (
50         d => wr,
51         l => auxL,
52         sel => writeReg
53     );
54
55     registros: for r in 0 to n-1 generate
56         reg: Registro Port map (
57             d => auxD,
58             q => auxQ(r),
59             clk => clk,
60             clr => clr,
61             l => auxL(r)
62         );
63     end generate;
64
65     mux1 : Multiplexor Port map (
66         cl0 => auxQ(0),
67         cl1 => auxQ(1),
68         cl2 => auxQ(2),
69         cl3 => auxQ(3),
70         cl4 => auxQ(4),
71         cl5 => auxQ(5),
72         cl6 => auxQ(6),
73         cl7 => auxQ(7),
74         cl8 => auxQ(8),
75         cl9 => auxQ(9),
76         cl10 => auxQ(10),
77         cl11 => auxQ(11),
78         cl12 => auxQ(12),
79         cl13 => auxQ(13),
80         cl14 => auxQ(14),
81         cl15 => auxQ(15),
82         sel => readReg1,
```

```
83         salida => auxReadData1
84     );
85     readData1 <= auxReadData1;
86
87     mux2 : Multiplexor Port map (
88         cl0 => auxQ(0),
89         cl1 => auxQ(1),
90         cl2 => auxQ(2),
91         cl3 => auxQ(3),
92         cl4 => auxQ(4),
93         cl5 => auxQ(5),
94         cl6 => auxQ(6),
95         cl7 => auxQ(7),
96         cl8 => auxQ(8),
97         cl9 => auxQ(9),
98         cl10 => auxQ(10),
99         cl11 => auxQ(11),
100        cl12 => auxQ(12),
101        cl13 => auxQ(13),
102        cl14 => auxQ(14),
103        cl15 => auxQ(15),
104        sel => readReg2,
105        salida => readData2
106    );
107
108    bs: BarrelShifter Port map(
109        dato => auxReadData1,
110        res => auxBS,
111        shamt => shamt,
112        direccion => dir
113    );
114
115    mux_2C: Mux2C Port map (
116        barrelShifter => auxBs,
117        write_data => writeData,
118        she => she,
119        sal => auxD
120    );
121 end Behavioral;
```

2. Código de simulación

2.1. Registro

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity tbRegistro is
5  end tbRegistro;
6
7  architecture Behavioral of tbRegistro is
8      component Registro is
9          Port ( d : in STD_LOGIC_VECTOR (15 downto 0);
10              q : out STD_LOGIC_VECTOR (15 downto 0);
11              clr, clk, l : in STD_LOGIC);
12      end component;
13
14      signal d : STD_LOGIC_VECTOR (15 downto 0);
15      signal q : STD_LOGIC_VECTOR (15 downto 0);
16      signal clr, clk, l : STD_LOGIC;
17  begin
18      reg : Registro Port map (
19          d => d,
20          q => q,
21          clk => clk,
22          clr => clr,
23          l => l
24      );
25
26      reloj : process begin
27          clk <= '0';
28          wait for 5 ns;
29          clk <= '1';
30          wait for 5 ns;
31      end process;
32
33      sim : process begin
34          clr <= '1';
35          wait for 40 ns;
36          clr <= '0';
37          l <= '1';
38          d <= x"1234";
39          wait for 10 ns;
40          l <= '0';
```

```
41         d <= x"8765";
42         wait;
43     end process;
44 end Behavioral;
```

2.2. Demultiplexor de 16 canales de salida

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity tbDemultiplexor is
5  end tbDemultiplexor;
6
7  architecture Behavioral of tbDemultiplexor is
8      component Demultiplexor is
9          Port ( d : in STD_LOGIC;
10              l : out std_logic_vector(15 downto 0);
11              sel : in STD_LOGIC_VECTOR (3 downto 0));
12      end component;
13
14      signal d : STD_LOGIC;
15      signal l : std_logic_vector(15 downto 0);
16      signal sel : STD_LOGIC_VECTOR (3 downto 0);
17  begin
18      demux: Demultiplexor Port map (
19          d => d,
20          l => l,
21          sel => sel
22      );
23
24      process begin
25          d <= '1';
26          sel <= "0000";
27          wait for 62 ns;
28
29          sel <= "0001";
30          wait for 62 ns;
31
32          sel <= "0010";
33          wait for 62 ns;
34
35          sel <= "0011";
36          wait for 62 ns;
```

```
37
38     sel <= "0100";
39     wait for 62 ns;
40
41     sel <= "0101";
42     wait for 62 ns;
43
44     sel <= "0110";
45     wait for 62 ns;
46
47     sel <= "0111";
48     wait for 62 ns;
49
50     sel <= "1000";
51     wait for 62 ns;
52
53     sel <= "1001";
54     wait for 62 ns;
55
56     sel <= "1010";
57     wait for 62 ns;
58
59     sel <= "1011";
60     wait for 62 ns;
61
62     sel <= "1100";
63     wait for 62 ns;
64
65     sel <= "1101";
66     wait for 62 ns;
67
68     sel <= "1110";
69     wait for 62 ns;
70
71     sel <= "1111";
72     wait;
73     end process;
74 end Behavioral;
```

2.3. Barrel-Shifter

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity tbBarrelShifter is
5  end tbBarrelShifter;
6
7  architecture Behavioral of tbBarrelShifter is
8      component BarrelShifter is
9          Port ( dato : in STD_LOGIC_VECTOR (15 downto 0);
10              res : out STD_LOGIC_VECTOR (15 downto 0);
11              shamt : in STD_LOGIC_VECTOR (3 downto 0);
12              direccion : in STD_LOGIC);
13      end component;
14
15      signal dato : STD_LOGIC_VECTOR (15 downto 0);
16      signal res : STD_LOGIC_VECTOR (15 downto 0);
17      signal shamt : STD_LOGIC_VECTOR (3 downto 0);
18      signal direccion : STD_LOGIC;
19  begin
20      barrel : BarrelShifter Port map (
21          dato => dato,
22          res => res,
23          shamt => shamt,
24          direccion => direccion
25      );
26
27      process begin
28          direccion <= '1'; --- izquierda
29          dato <= "0000000010010111";
30          shamt <= "0011";
31          wait for 500 ns;
32          direccion <= '0'; --- derecha
33          dato <= "0000000010010001";
34          shamt <= "0100";
35          wait;
36      end process;
37  end Behavioral;
```

2.4. Archivo de Registros

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.numeric_std.all;
4  use STD.textio.all;
5  use IEEE.std_logic_textio.all;
6
7  entity test_bench is
8  end test_bench;
9
10 architecture Behavioral of test_bench is
11     component ArchivoRegistros is
12         Port ( wr, dir, she, clk, clr : in STD_LOGIC;
13             writeReg, readReg1, readReg2, shamt : in STD_LOGIC_VECTOR (3
14                 ↪ downto 0);
15             writeData : in STD_LOGIC_VECTOR (15 downto 0);
16             readData1, readData2 : out STD_LOGIC_VECTOR (15 downto 0));
17     end component;
18
19     signal wr, dir, she, clk, clr : STD_LOGIC;
20     signal writeReg, readReg1, readReg2, shamt : STD_LOGIC_VECTOR (3 downto
21         ↪ 0);
22     signal writeData, readData1, readData2 : STD_LOGIC_VECTOR (15 downto 0);
23 begin
24     ar: ArchivoRegistros Port map (
25         wr => wr,
26         she => she,
27         dir => dir,
28         clk => clk,
29         clr => clr,
30         writeReg => writeReg,
31         readReg1 => readReg1,
32         readReg2 => readReg2,
33         shamt => shamt,
34         writeData => writeData,
35         readData1 => readData1,
36         readData2 => readData2
37     );
38
39     reloj : process begin
40         clk <= '0';
41         wait for 5 ns;
42         clk <= '1';
```

```

41     wait for 5 ns;
42 end process;
43
44 process
45     file arch_res : text;    --Apuntadores tipo
        ↳ txt
46     variable linea_res : line;
47     variable var_read_data1 : STD_LOGIC_VECTOR (15 downto 0);
48     variable var_read_data2 : STD_LOGIC_VECTOR (15 downto 0);
49
50     file arch_en : text; --Apuntadores tipo txt
51     variable linea_en: line;
52     variable var_write : STD_LOGIC_VECTOR (15 downto 0);
53     variable var_wr, var_she, var_dir, var_clr : STD_LOGIC;
54     variable var_write_reg, var_read_reg1, var_read_reg2, var_shamt :
        ↳ STD_LOGIC_VECTOR (3 downto 0);
55     variable var_write_data : STD_LOGIC_VECTOR (15 downto 0);
56     variable cadena : string (1 to 5);
57 begin
58     --- RR1 RR2 SHAMT WREG WD CLR WR SHE DIR
59     file_open(arch_en, "Estimulos.txt", READ_MODE);
60
61     --- RR1 RR2 SHAMT WREG WD WR SHE DIR RD1 RD2
62     file_open(arch_res, "Resultado.txt", WRITE_MODE);
63
64     cadena := " RR1";
65     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "readReg1"
66     cadena := " RR2";
67     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "readReg2"
68     cadena := "SHAMT";
69     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "shamt"
70     cadena := " WREG";
71     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "writeReg"
72     cadena := " WD";
73     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "writeData"
74     cadena := " WR";
75     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
        ↳ "WR"
76     cadena := " SHE";

```



```
77     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
      ↪ "SHE"
78     cadena := "  DIR";
79     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
      ↪ "DIR"
80     cadena := "  RD1";
81     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
      ↪ "readData1"
82     cadena := "  RD2";
83     write(linea_res, cadena, right, cadena'LENGTH+1);--ESCRIBE LA cadena
      ↪ "readData2"
84
85     writeline(arch_res, linea_res);-- escribe la linea en el archivo
86
87     wait for 100 ns;
88     for i in 0 to 11 loop
89         readline(arch_en, linea_en); -- lee una linea completa
90         --- RR1 RR2 SHAMT WREG WD CLR WR SHE DIR
91
92         --Lee readReg1
93         read(linea_en, var_read_reg1);
94         readReg1 <= var_read_reg1;
95
96         --Lee readReg2
97         read(linea_en, var_read_reg2);
98         readReg2 <= var_read_reg2;
99
100        --Lee shamt
101        read(linea_en, var_shamt);
102        shamt <= var_shamt;
103
104        --Lee writeReg
105        read(linea_en, var_write_reg);
106        writeReg <= var_write_reg;
107
108        --Lee writeData
109        read(linea_en, var_write_data);
110        writeData <= var_write_data;
111
112        --Lee clr
113        read(linea_en, var_clr);
114        clr <= var_clr;
115
116        --Lee wr
```


```

117         read(linea_en, var_wr);
118         wr <= var_wr;
119
120         --Lee she
121         read(linea_en, var_she);
122         she <= var_she;
123
124         --Lee dir
125         read(linea_en, var_dir);
126         dir <= var_dir;
127
128         wait until rising_edge(clk); --ESPERA AL FLANCO DE SUBIDA
129         var_read_data1 := readData1;
130         var_read_data2 := readData2;
131         --- RR1 RR2 SHAMT WREG WD WR SHE DIR RD1 RD2
132         Hwrite(linea_res, var_read_reg1, right, 5);--ESCRIBE EL CAMPO
133         ↪ RR1
134         Hwrite(linea_res, var_read_reg2, right, 6);--ESCRIBE EL CAMPO
135         ↪ RR2
136         Hwrite(linea_res, var_shamt, right, 6);--ESCRIBE EL CAMPO shamt
137         Hwrite(linea_res, var_write_reg, right, 5);--ESCRIBE EL CAMPO
138         ↪ WREG
139         Hwrite(linea_res, var_write_data, right, 8);--ESCRIBE EL CAMPO
140         ↪ WD
141         write(linea_res, var_wr, right, 7);--ESCRIBE EL CAMPO WR
142         write(linea_res, var_she, right, 5);--ESCRIBE EL CAMPO SHE
143         write(linea_res, var_dir, right, 6);--ESCRIBE EL CAMPO DIR
144         Hwrite(linea_res, var_read_data1, right, 6);--ESCRIBE EL CAMPO
145         ↪ RD1
146         Hwrite(linea_res, var_read_data2, right, 6);--ESCRIBE EL CAMPO
147         ↪ RD2
148
149         writeline(arch_res, linea_res);-- escribe la linea en el archivo
150     end loop;
151     file_close(arch_en); -- cierra el archivo
152     file_close(arch_res); -- cierra el archivo
153     wait;
154 end process;
155 end Behavioral;


```

3. Simulación

3.1. Registro

 


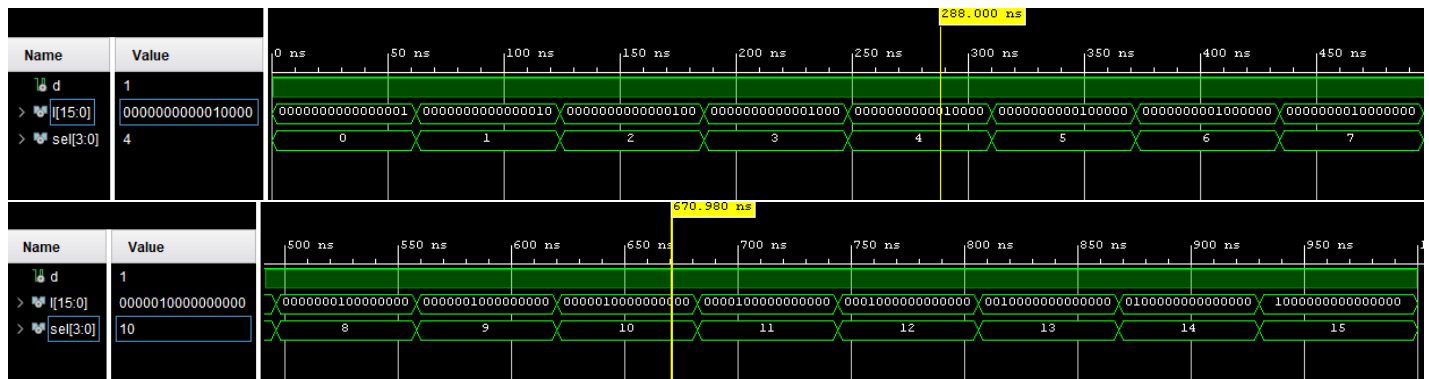3.2. Demultiplexor de 16 canales de salida




3.3. Barrel-Shifter

3.3.1. Corrimiento a la izquierda

 


3.3.2. Corrimiento a la derecha

 

3.4. Archivo de Registros

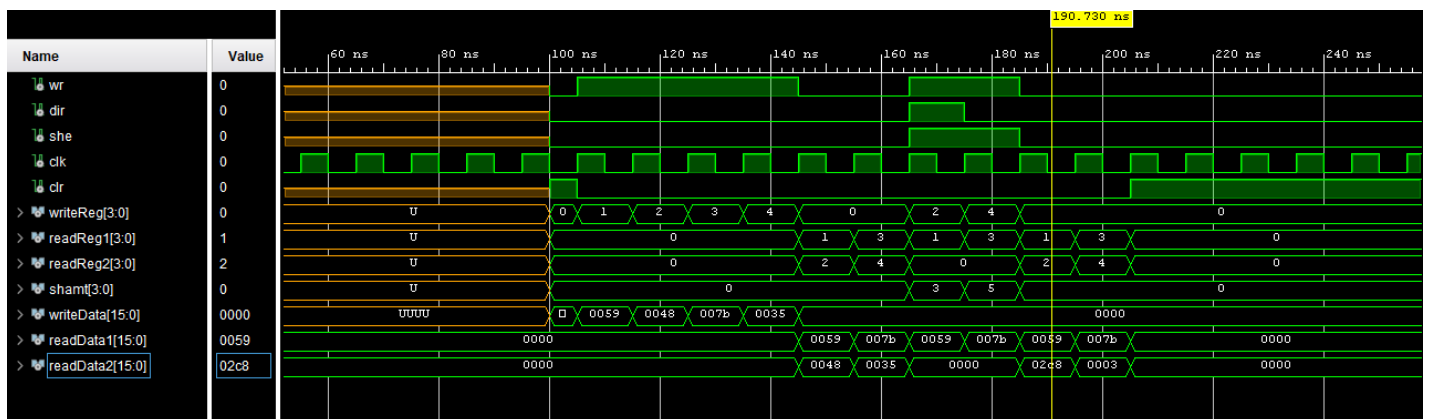1. Reset
2. Banco[1] = 89
3. Banco[2] = 72
4. Banco[3] = 123
5. Banco[4] = 53
6. Leer Banco[1] y Banco[2]
7. Leer Banco[3] y Banco[4]
8. Banco[2] = Banco[1] \ll 3
- »9. Banco[4] = Banco[3] \gg 5
10. Leer Banco[1] y Banco[2]
11. Leer Banco[3] y Banco[4]
12. Reset



3.4.1. Archivo entrada: Estimulos.txt

```

1  --- RR1 RR2 SHAMT WREG WD CLR WR SHE DIR
2  0000 0000 0000 0000 0000000000000000 1 0 0 0
3  0000 0000 0000 0001 00000000001011001 0 1 0 0
4  0000 0000 0000 0010 00000000001001000 0 1 0 0
5  0000 0000 0000 0011 00000000001111011 0 1 0 0
6  0000 0000 0000 0100 0000000000110101 0 1 0 0
7  0001 0010 0000 0000 0000000000000000 0 0 0 0
8  0011 0100 0000 0000 0000000000000000 0 0 0 0
9  0001 0000 0011 0010 0000000000000000 0 1 1 1
10 0011 0000 0101 0100 0000000000000000 0 1 1 0
11 0001 0010 0000 0000 0000000000000000 0 0 0 0
12 0011 0100 0000 0000 0000000000000000 0 0 0 0
13 0000 0000 0000 0000 0000000000000000 1 0 0 0

```


3.4.2. Archivo salida: Resultados.txt

	RR1	RR2	SHAMT	WREG	WD	WR	SHE	DIR	RD1	RD2
1										
2	0	0	0	0	0000	0	0	0	0000	0000
3	0	0	0	1	0059	1	0	0	0000	0000
4	0	0	0	2	0048	1	0	0	0000	0000
5	0	0	0	3	007B	1	0	0	0000	0000
6	0	0	0	4	0035	1	0	0	0000	0000
7	1	2	0	0	0000	0	0	0	0059	0048
8	3	4	0	0	0000	0	0	0	007B	0035
9	1	0	3	2	0000	1	1	1	0059	0000
10	3	0	5	4	0000	1	1	0	007B	0000
11	1	2	0	0	0000	0	0	0	0059	02C8
12	3	4	0	0	0000	0	0	0	007B	0003
13	0	0	0	0	0000	0	0	0	0000	0000


4. Diagramas RTL

4.1. Análisis RTL


4.1.1. Registro

 


4.1.2. Multiplexor de 16 canales

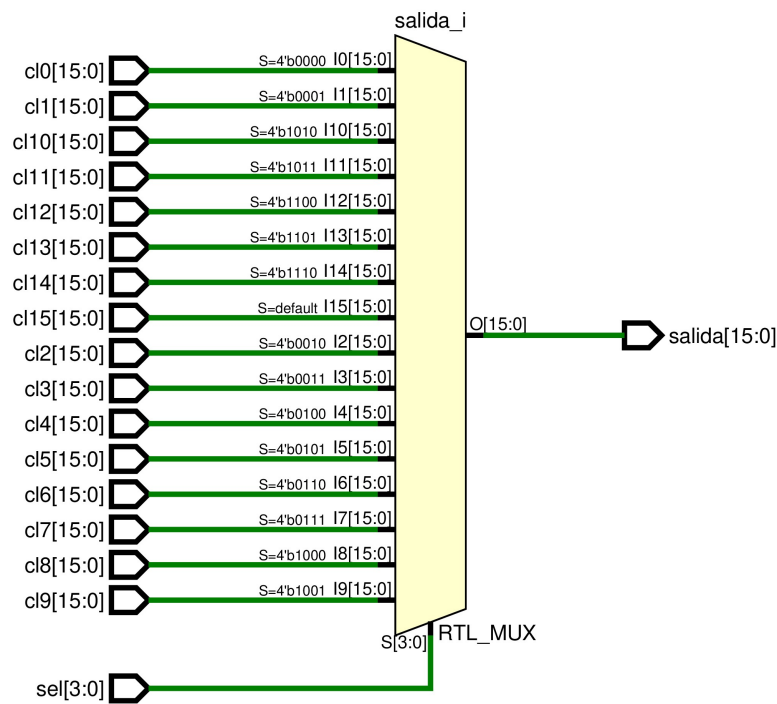

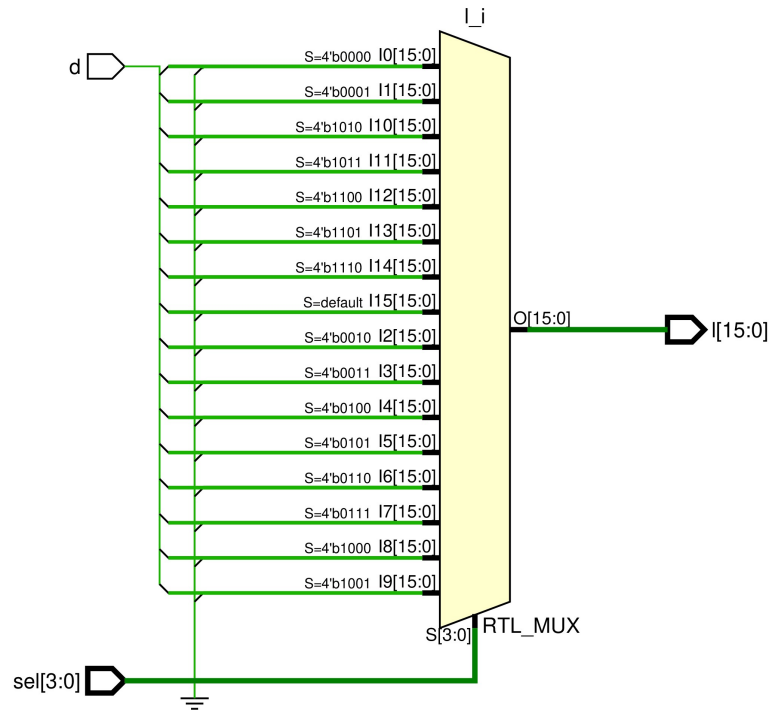
4.1.3. Demultiplexor de 16 canales de salida



4.1.4. Barrel-Shifter

 

4.1.5. Multiplexor de 2 canales

 

4.1.6. Archivo de Registros

Diagrama comprimido



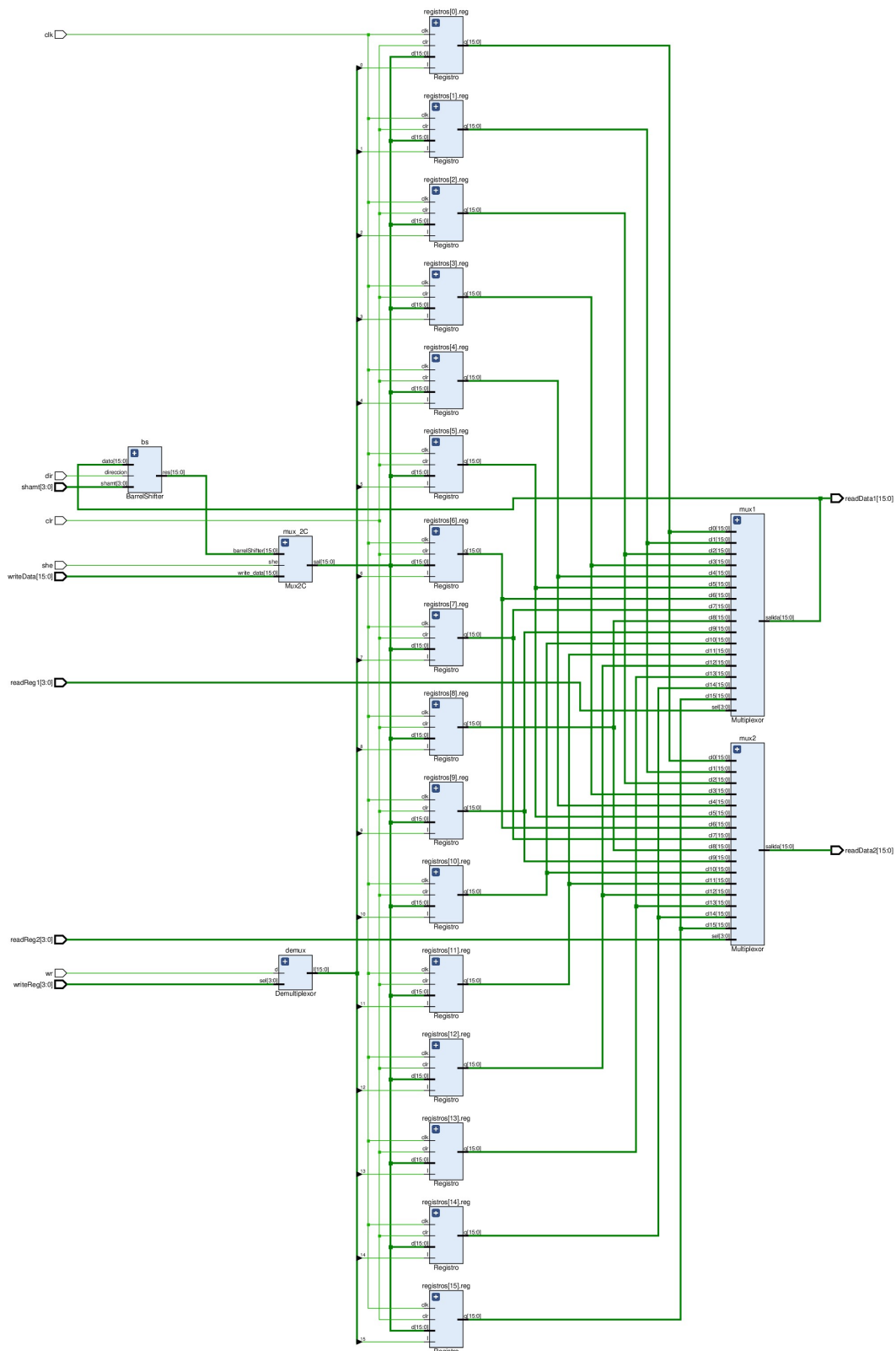


Diagrama expandido

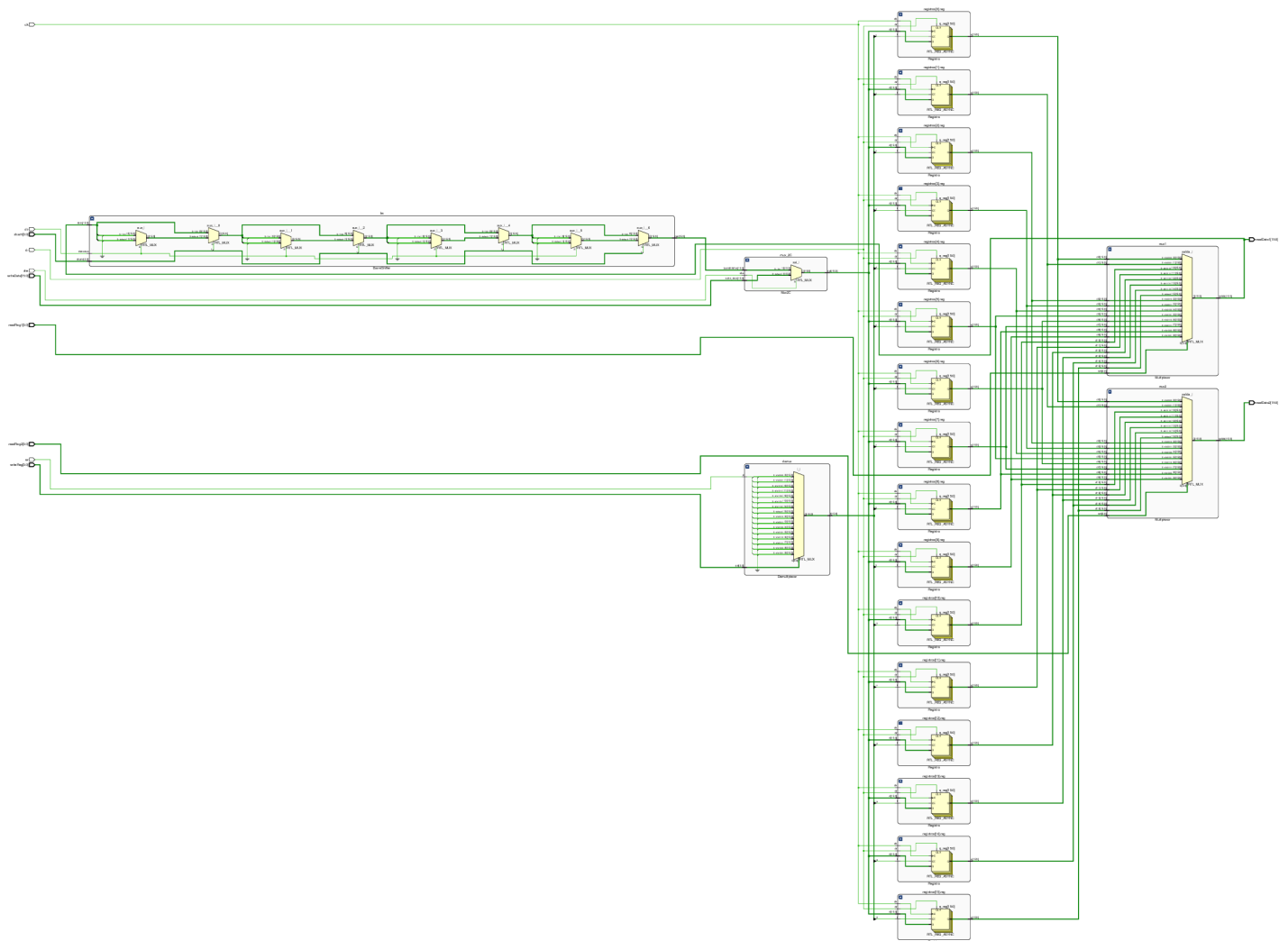


4.2. Synthesis


4.2.1. Registro

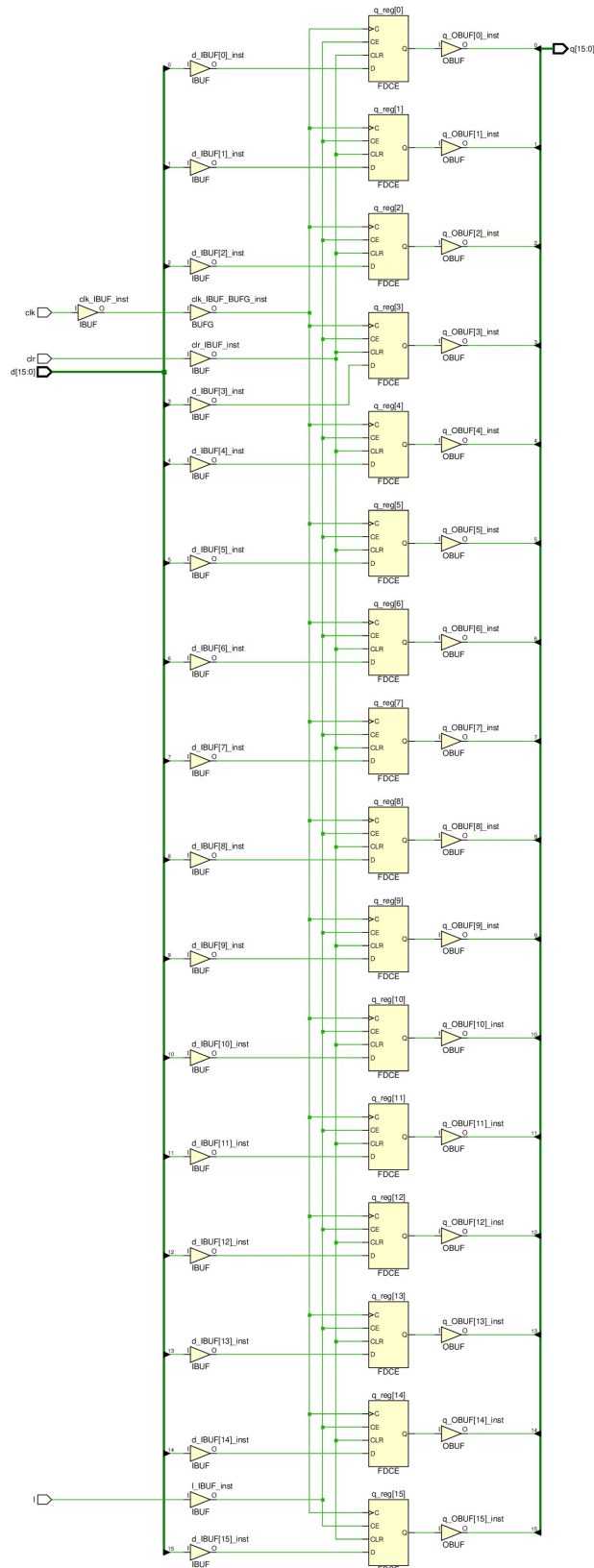


4.2.2. Multiplexor de 16 canales

 

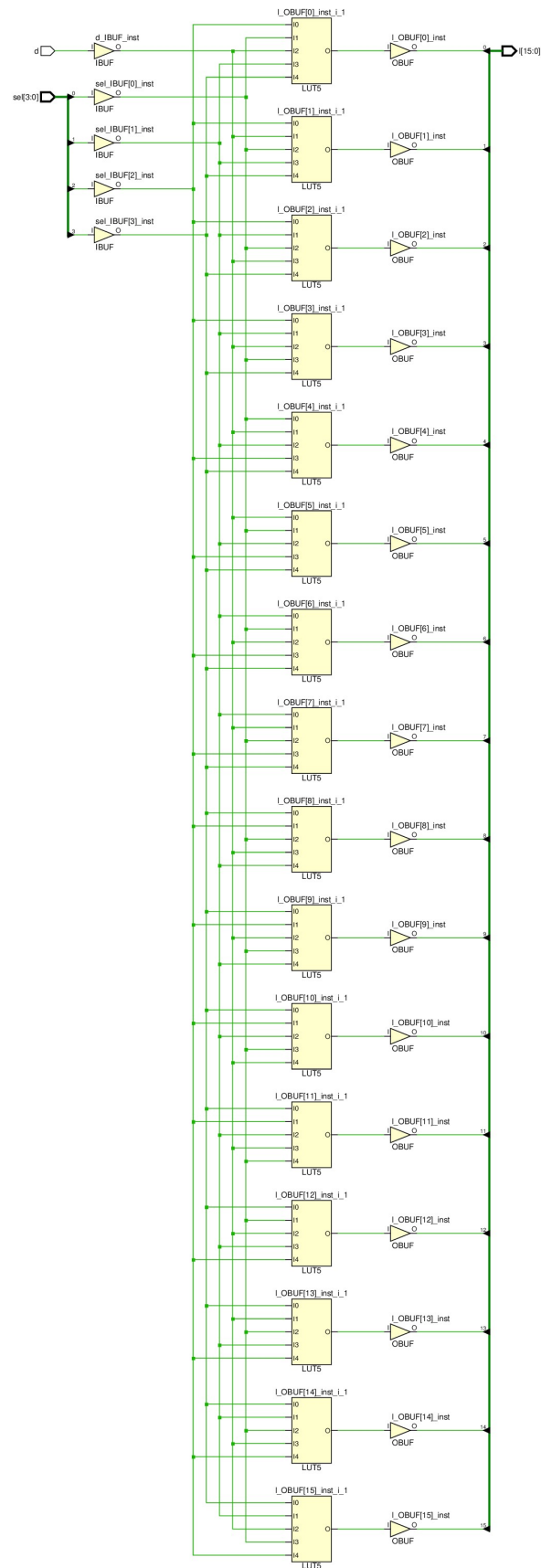
4.2.3. Demultiplexor de 16 canales de salida



4.2.4. Barrel-Shifter

 

4.2.5. Multiplexor de 2 canales

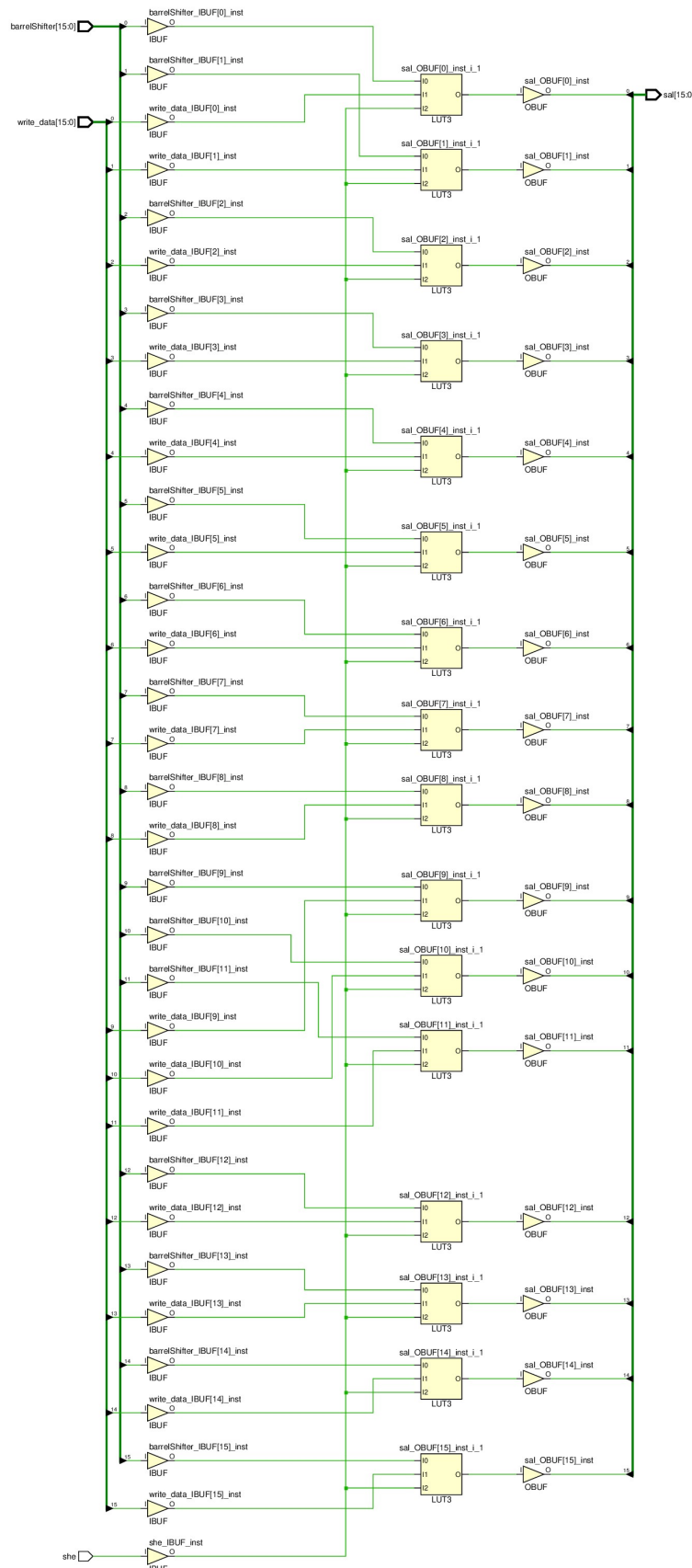

4.2.6. Archivo de Registros

Diagrama comprimido

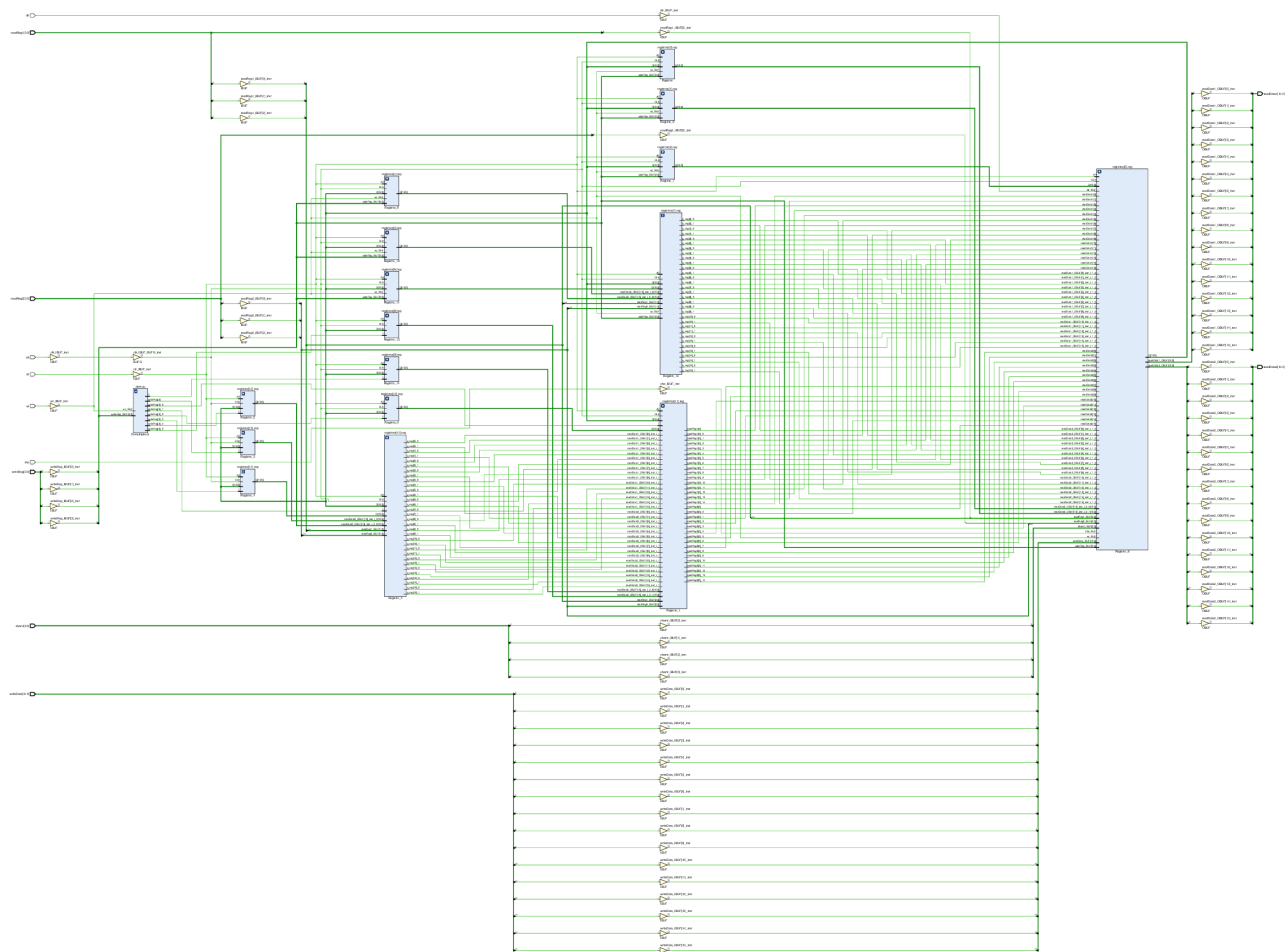


Diagrama expandido

